



Electrical and Computer Engineering Department

Written by:

Group K

Brandon Contreras

Daniele Ricciardelli

ECE 2200L:

Experiment Number 6

Bipolar Junction Transistor Biasing Circuits and Bias Point Stability

Represented to

Professor Mostafa Yazdy

Fall 2024

Thursday

October 10th, 2024


Background Information:

PNP transistor, also known as a Bipolar Junction Transistor (BJT), is a semiconductor device used in various applications. One of its primary functions is to amplify AC signals. To ensure stable operation, a BJT must be properly biased to maintain consistent values regardless of β .

Objective:

To study and experiment on three types of DC biasing circuits for BJTs, and compare the stability of the bias point in these circuits.

Pre-Lab:

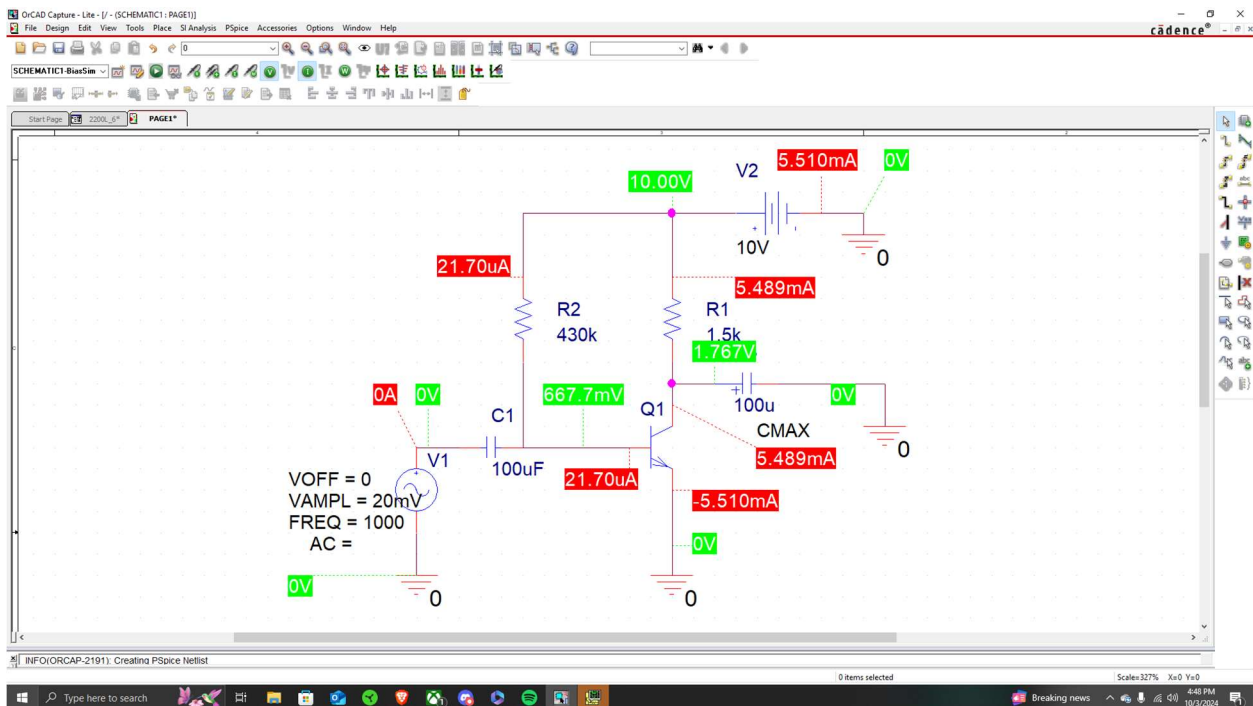

A)

$$I_B = \frac{V_{cc} - V_{be}}{R_B} = \frac{10 - V_{be}}{R_B} \quad \text{Assume } V_{be} = 0.7$$

$$I_C = \beta \cdot I_B = \frac{V_{cc} - 10}{R_C}$$

$$I_C = \beta \cdot I_B = \frac{V_{cc} - 10}{R_C}$$

$$I_B = \frac{10 - 0.7}{430 \times 10^3} \approx 22 \mu A$$

$$I_C = \beta \cdot I_B = 3.244 \text{ mA}$$

$$10 - I_C R_C - V_{CE} = 0 \Rightarrow V_{CE} = 10 - (3.244 \times 10^{-3})(1.5 \times 10^3)$$

$$V_{CE} = 5.1337 \text{ V} \approx 5.13 \text{ V}$$

$$I_B = \frac{10 - 0.7}{430 \times 10^3} = 22 \mu A$$

$$I_C = \beta \cdot I_B = 4.326 \text{ mA}$$

$$V_{CE} = 10 - (4.326 \times 10^{-3})(1.5 \times 10^3) = 3.512 \text{ V} \approx 3.5 \text{ V}$$

B)

$$\text{Percentage Change} \rightarrow \frac{\text{New Value} - \text{Old Value}}{\text{Old Value}} \times 100$$

$$I_C \rightarrow \frac{4.33 \text{ mA} - 3.24 \text{ mA}}{3.24 \text{ mA}} \times 100 \approx 33.64\%$$

$$V_{CE} \rightarrow \frac{5.14 - 3.5}{5.14} \times 100 = 31.91\%$$

c)

$$V_{eq} = 10 \cdot \frac{3.3k}{15k + 3.3k} = 1.80328 V$$

$$R_{eq} = \frac{15k \cdot 3.3k}{15k + 3.3k} = 2.70492 k\Omega$$

$$\text{Assume } V_{BE} = 0.7$$

$$\text{KVL: } 1.8 - 2.7kI_B - V_{BE} - 200I_E = 0$$

$$I_E = I_B + I_C \Rightarrow I_E = I_B(1 + \beta)$$

$$1.8 - 2.7kI_B - 0.7 - 200I_B(1 + \beta) = 0$$

$$I_B = \frac{1.10328}{32.9k} = 33.529 \mu A \approx 33.5 \mu A$$

$$I_C = \beta I_B = 5.029 mA \approx 5.03 mA$$

$$I_E = I_B + I_C = 5.063 mA$$

$$\text{KVL: } 10 - 820I_C = V_{CE} - 200I_E = 0$$

$$V_{CE} = 10 - 820(5.03 mA) - 200(5.063 mA) = 4.8633 V \approx 4.86 V$$

$$I_B = 25.7 \mu A$$

$$I_E = I_B + I_C = 5.169 mA$$

$$I_C = \beta I_B = 5.143 mA$$

$$V_{CE} = 10 - 820(5.143 mA) - 200(5.169 mA) = 4.749 V$$

$$I_C \text{ percent change} \approx 2.26\%$$

$$V_{CE} \text{ percent change} \approx 2.35\%$$

Proof of verified work:

(c)

$V_{ce} = 10 - \frac{3.3k}{15k + 3.3k} \cdot 10 = 1.80328V$
 $R_{eq} = \frac{15k \cdot 3.3k}{15k + 3.3k} = 2.70492$
 Assume $V_{ce} = 0.7$

$1.8 - 2.7k I_B - V_{ce} - 200 I_E = 0$
 $I_E = I_B + I_C \rightarrow I_B(1 + \beta)$
 $1.8 - 2.7k I_B - 0.7 - 200 I_B(1 + \beta) = 0$

For $\beta = 150$

$I_B = \frac{1.10328}{32.9k} = 33.529 \mu A$
 $\approx 33.5 \mu A$ (KVL)
 $I_C = \beta I_B = 5.029 mA$
 $\approx 5.03 mA$
 $I_E = I_B + I_C = 5.063 mA$

$1.8 - I_B(2.7k + 200 + 200\beta) - 0.7 = 0$
 $10 - 820 I_C - V_{ce} - 200 I_E = 0$
 $V_{ce} = 10 - 820(5.03 mA) - 200(5.063 mA)$
 $= 4.8633V$
 $\approx 4.86V$

For $\beta = 100$

$I_B = 25.7 \mu A$
 $I_C = \beta I_B = 5.143 mA$
 $I_E = I_B + I_C = 5.169 mA$


$V_{ce} = 10 - 820(5.143 mA) - 200(5.169 mA) = 4.749V$

Percent change


I_C percent change $\approx 2.26\%$
 V_{ce} percent change $\approx 2.35\%$

Lab Report:


1. Figure 1:

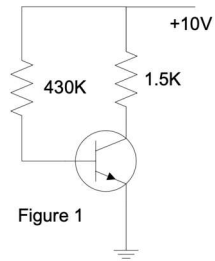

2. Figure 2:

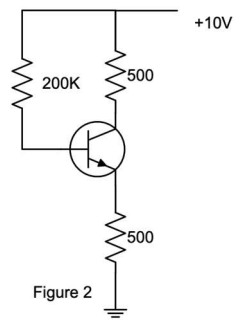

3. Figure 3:

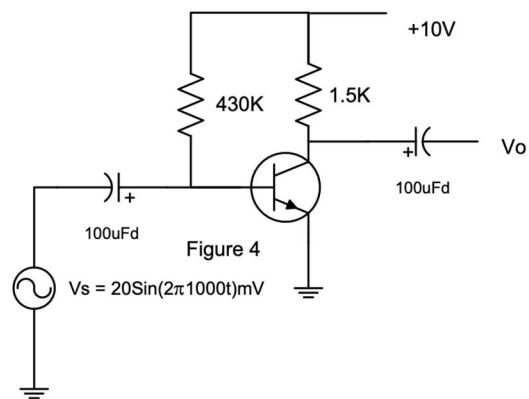

Data tables:




Q1=3904
Q2=2222

Figure1	Vb	Vc	Ic(mA)	Ib(mA)	Beta
Q1	0.72	4.74E+00	3.51E+00	0.021581	1.62E+02
Q2	0.67	1.88E+00	5.41E+00	0.021698	2.49E+02

Figure2	Vb	Vc	Ve	Ic(mA)	Ib(uA)	Beta
Q1	3.44	7.25	2.75	5.5	50.94	1.08E-01
Q2	4.28	6.35	3.64	7.3	43.62	1.67E-01

Figure3	Vb	Vc	Ve	Ic(mA)	Ib(uA)	Beta
Q1	1.74	5.80E+00	1.04	5.12E+00	32.63	1.57E-01
Q2	1.76	5.48	1.115	5.51E+00	28.3	1.95E-01

Constructed circuits:

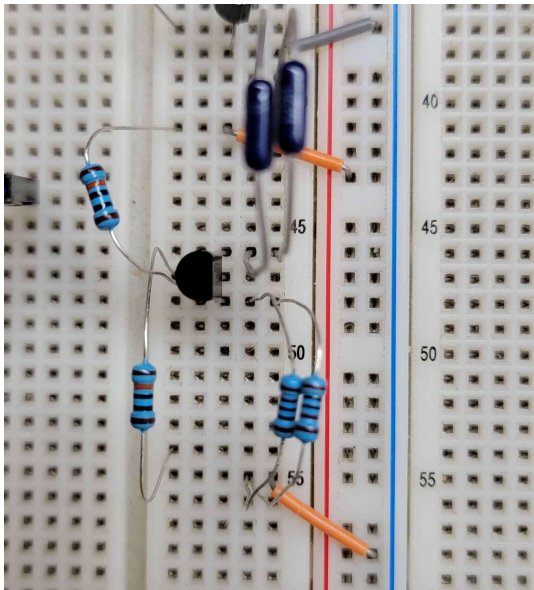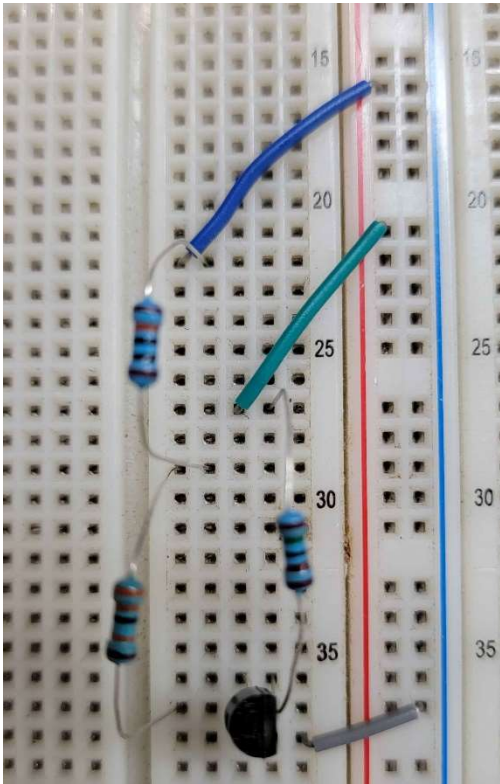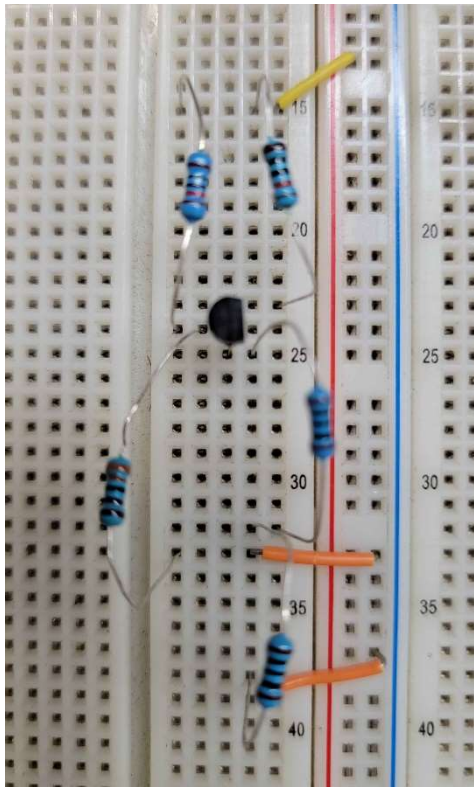

Conclusion:

In this Experiment, we build the three circuits physically in the lab. Each circuit had different number of resistors to see which one will give us the most stability regardless of the value of β . In the last figure, we created an AC Amplifier using a BJT and 4 resistors, and 2 coupling capacitors. We also plotted V_{in} and V_{out} vs time, as well as V_s and V_{in} vs time on the oscilloscope to calculate the gain.

Post Lab:

1. For the circuits in Figures 1, 2 and 3, calculate and tabulate I_C , I_B and Beta for two different BJT's. → Done in the lab report chart
2. Compare the measurements for V_{be} , V_{ce} , I_C and I_B (in Figure 3) to the simulation results from prelab of experiment 5 (the same circuit).

After Implementing the above figure on the breadboard, we got:

$$V_{BE} = 0.7V$$

$$V_E = 1.08V$$

$$V_C = 5.5V$$

$$I_{15K} \approx 10I_B = \frac{V_{CC} - V_B}{15k\Omega} = \frac{10 - 1.7}{15k} = 5.53 \times 10^{-4} A = 0.55 mA$$

- $I_B = 55.3 \mu A$
- $I_C = \frac{V_{CC} - V_C}{820\Omega} = \frac{10 - 5.5}{820} = 5.49 mA$
- $I_E = \frac{1.08V}{200\Omega} = 5.4 mA$
- $I_C \approx I_E$