



Electrical and Computer Engineering Department

Group K:

Brandon Contreras

Daniele Ricciardelli

ECE 2200L

Experiment Number 3

Current-Voltage Characteristics of the Zener Diode

Represented to

Professor Mosatfa ,Yazdy

Fall 2024

Thursday



September 19, 2024

Objective:

The objective of this experiment is to thoroughly analyze the current-voltage (I-V) relationship of Zener diodes, focusing on key parameters such as reverse saturation current and the diode's ideality factor. By plotting the I-V characteristics, we can observe the diode's behavior under different voltage conditions, particularly in the reverse breakdown region. Additionally, the XY mode of the oscilloscope will be utilized to visually display these characteristics, allowing for real-time monitoring and a more precise understanding of the Zener diode's performance in both forward and reverse bias modes. This analysis will provide insights into the diode's efficiency and reliability in various applications.

Prelab:

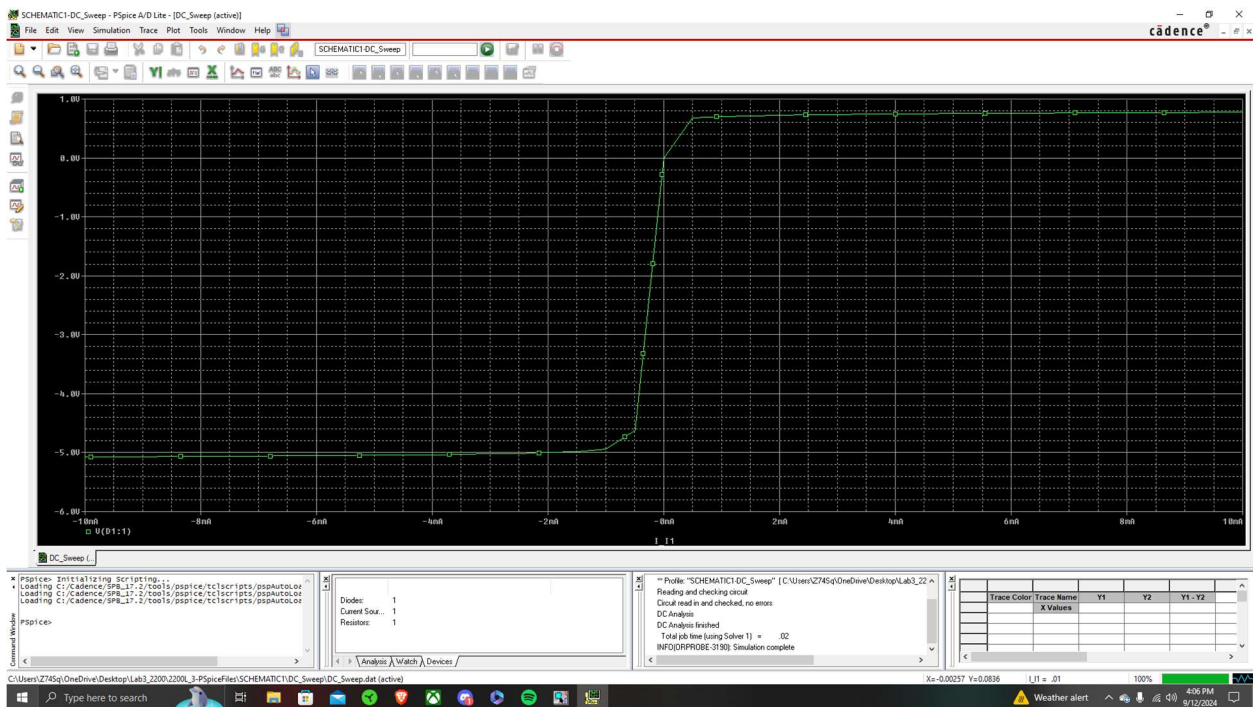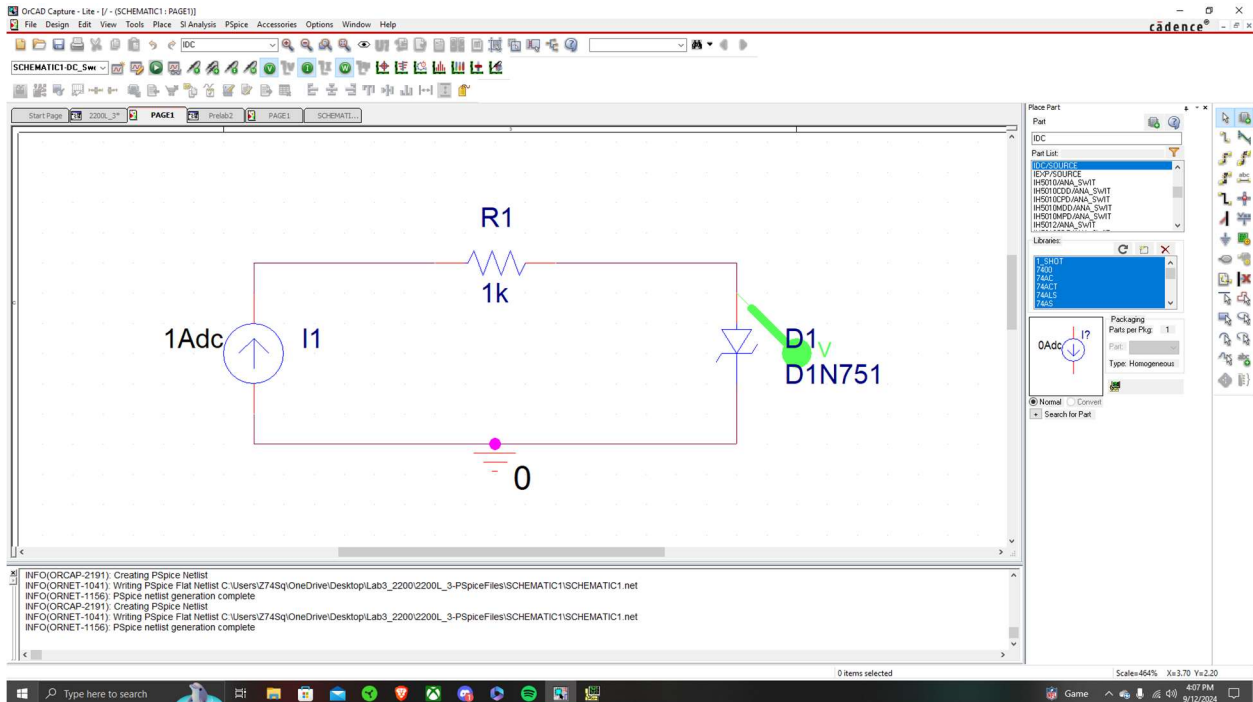Run DC Sweep Simulation to find the I-V characteristic of a Zener Diode (1N751) (-10mA to +10mA).



Measurements:

1- Given


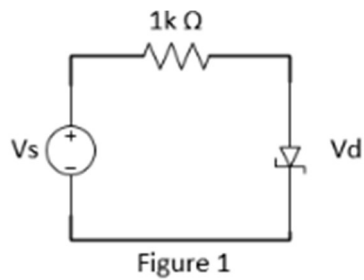


Table 1.1

R				
1047.4000 Ω				
V_s	V_d	V_r	I_d	
0.0000	0.0006	-0.0006	0.0000	
0.3300	0.3300	0.0000	0.0000	
0.6600	0.6361	0.0239	0.0000	
1.0000	0.7002	0.2998	0.0003	
2.0000	0.7376	1.2624	0.0012	
4.0000	0.7625	3.2375	0.0031	
6.0000	0.7756	5.2244	0.0050	
8.0000	0.6200	7.3800	0.0070	
10.0000	0.6200	9.3800	0.0090	

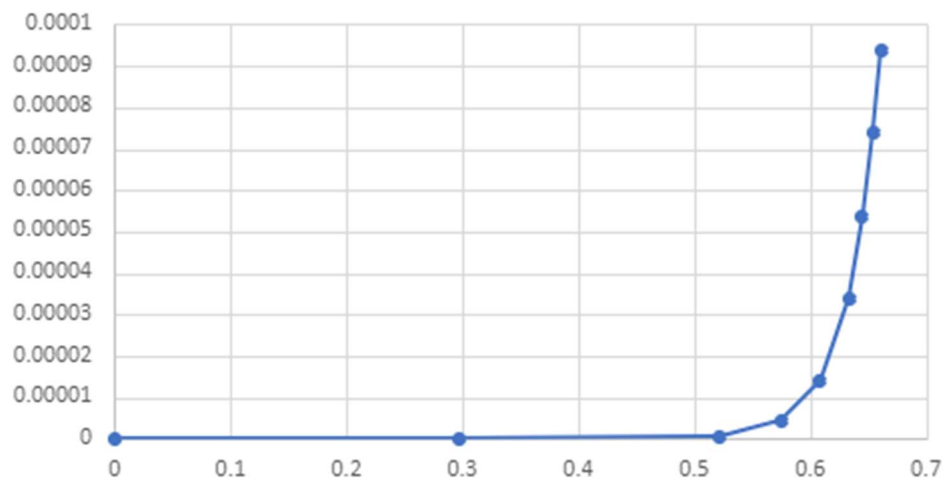I_d vs Characteristic Curve in Forward Bias



2- Given


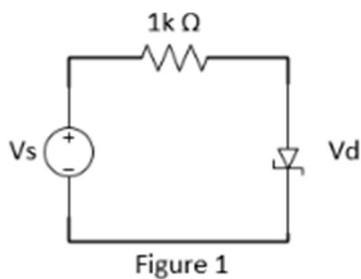


Table 1.2

R				
100950.0000				
Vs	Vd	Vr	Id	-
0.0000	0.0006	-0.0006	0.00000001	
1.0000	0.9910	0.0090	0.00000009	
2.0000	1.9692	0.0308	0.00000031	
3.0000	2.7605	0.2395	0.00000237	
4.0000	3.1990	0.8010	0.00000793	
5.0000	3.4556	1.5444	0.00001530	
6.0000	3.6295	2.3705	0.00002348	

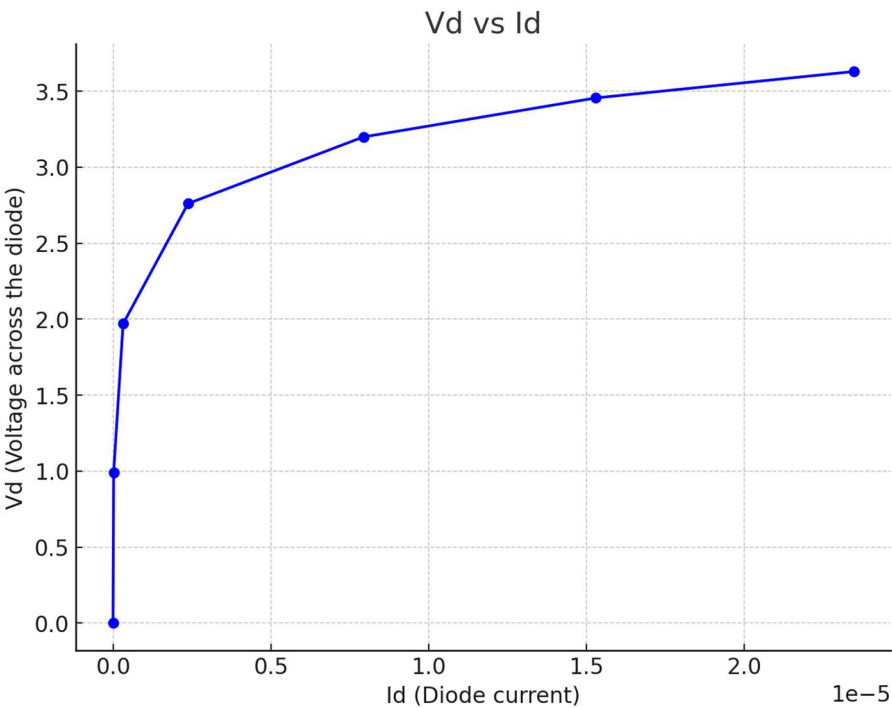

3- Given

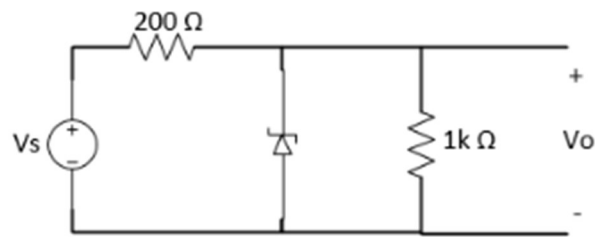


Figure 3

Schematic


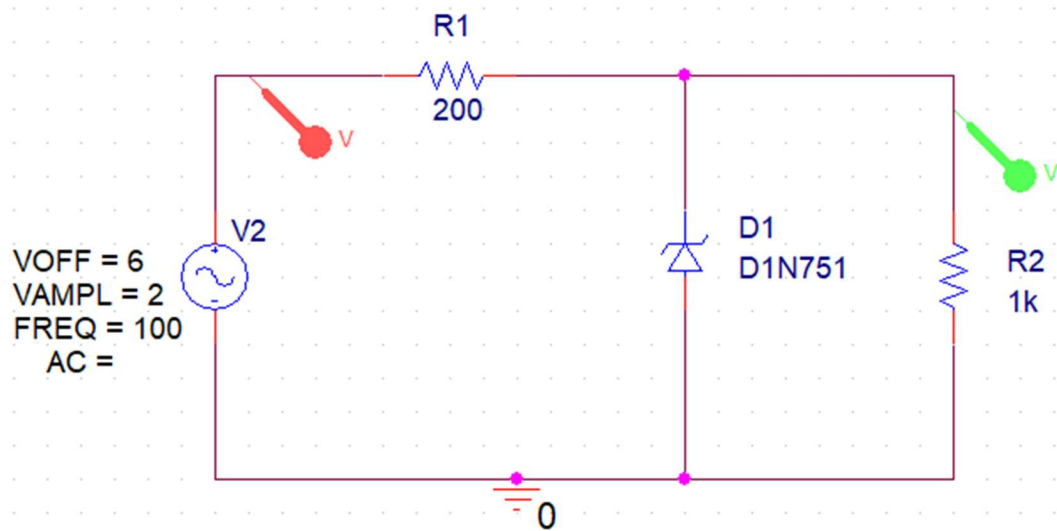



Figure 3:

Vd.t Vs Id

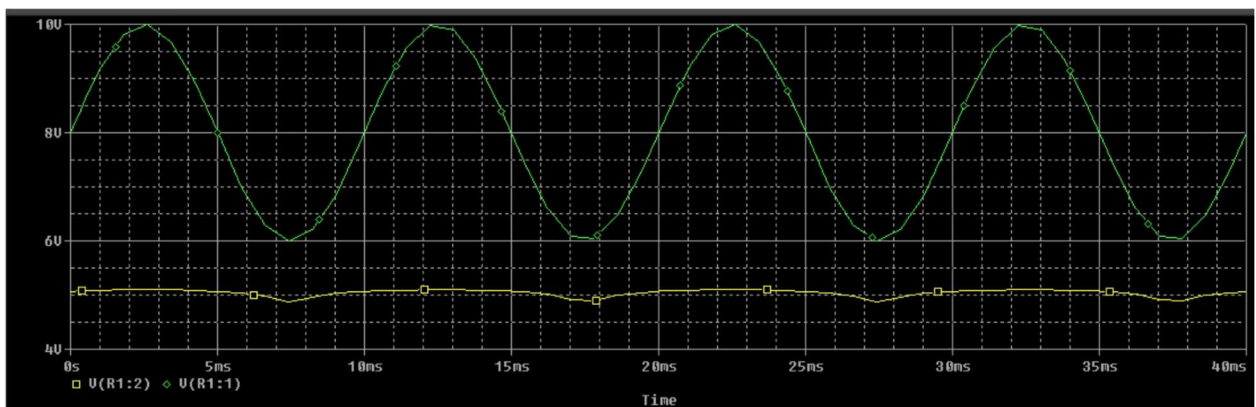

Data Analysis:

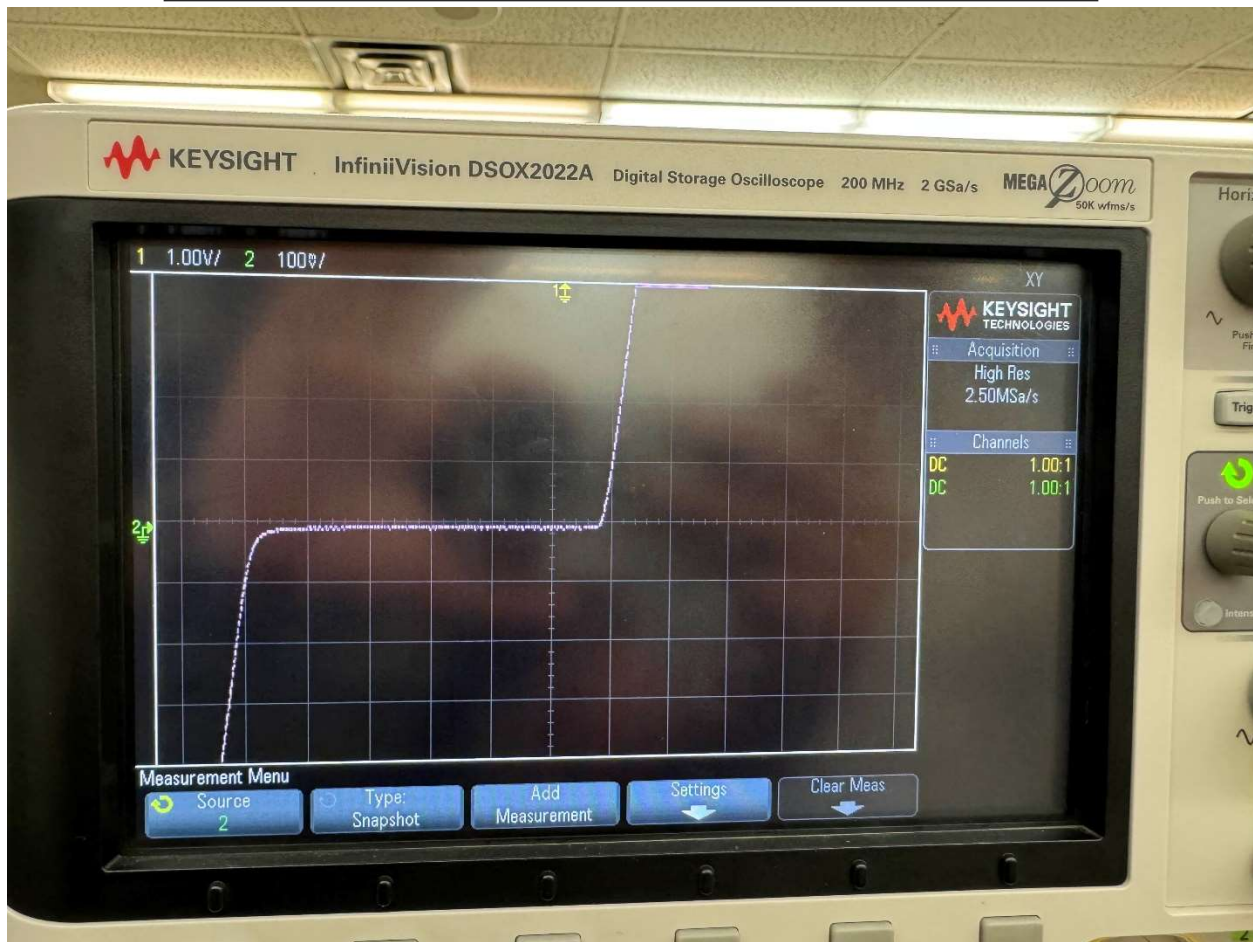
Plot forward and reverse I_a vs. V_a from the data obtained from your measurements from figure 1 and figure 2.




Circuit pictures

BELOW


Part 1:

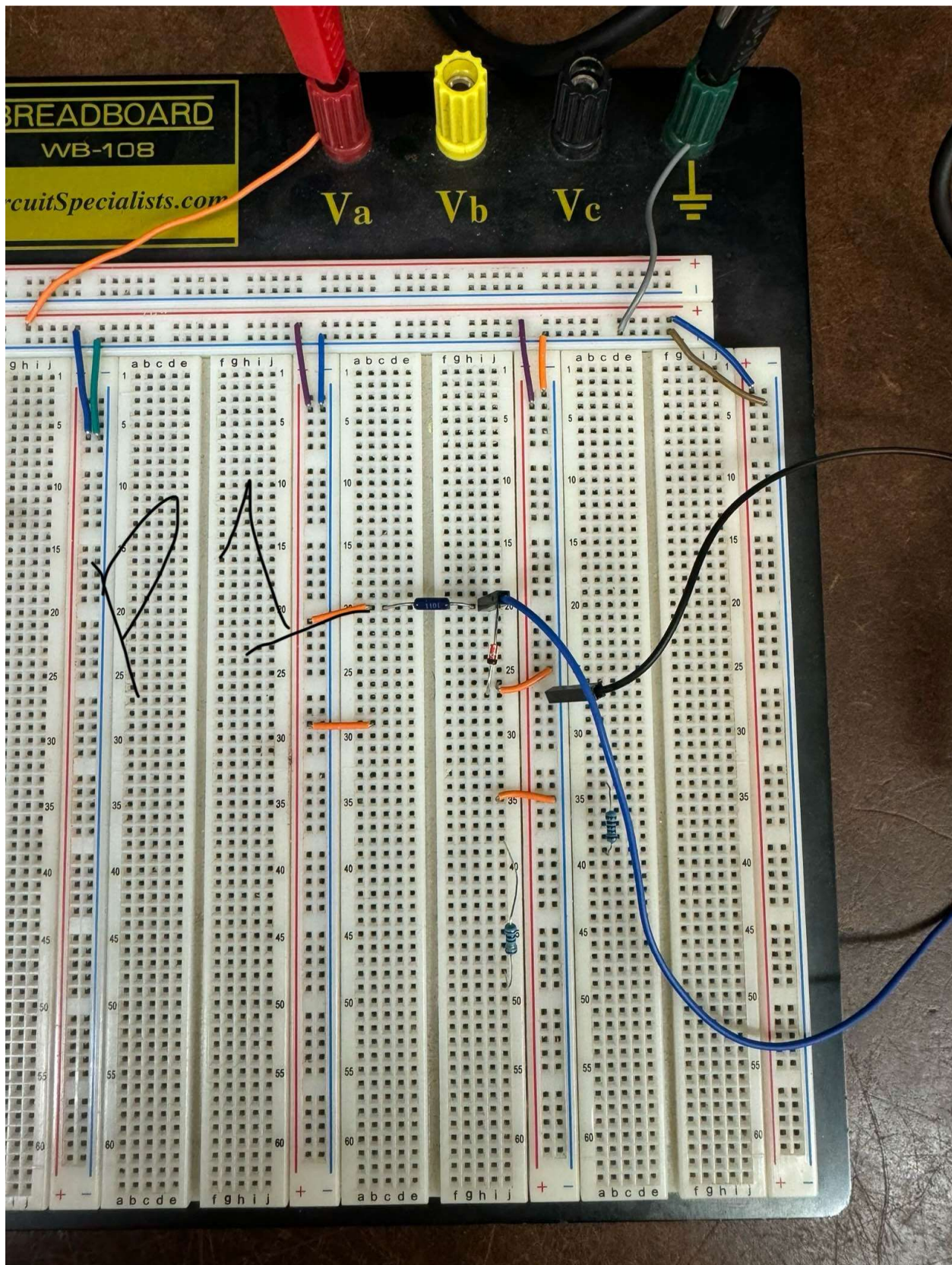

Part 2

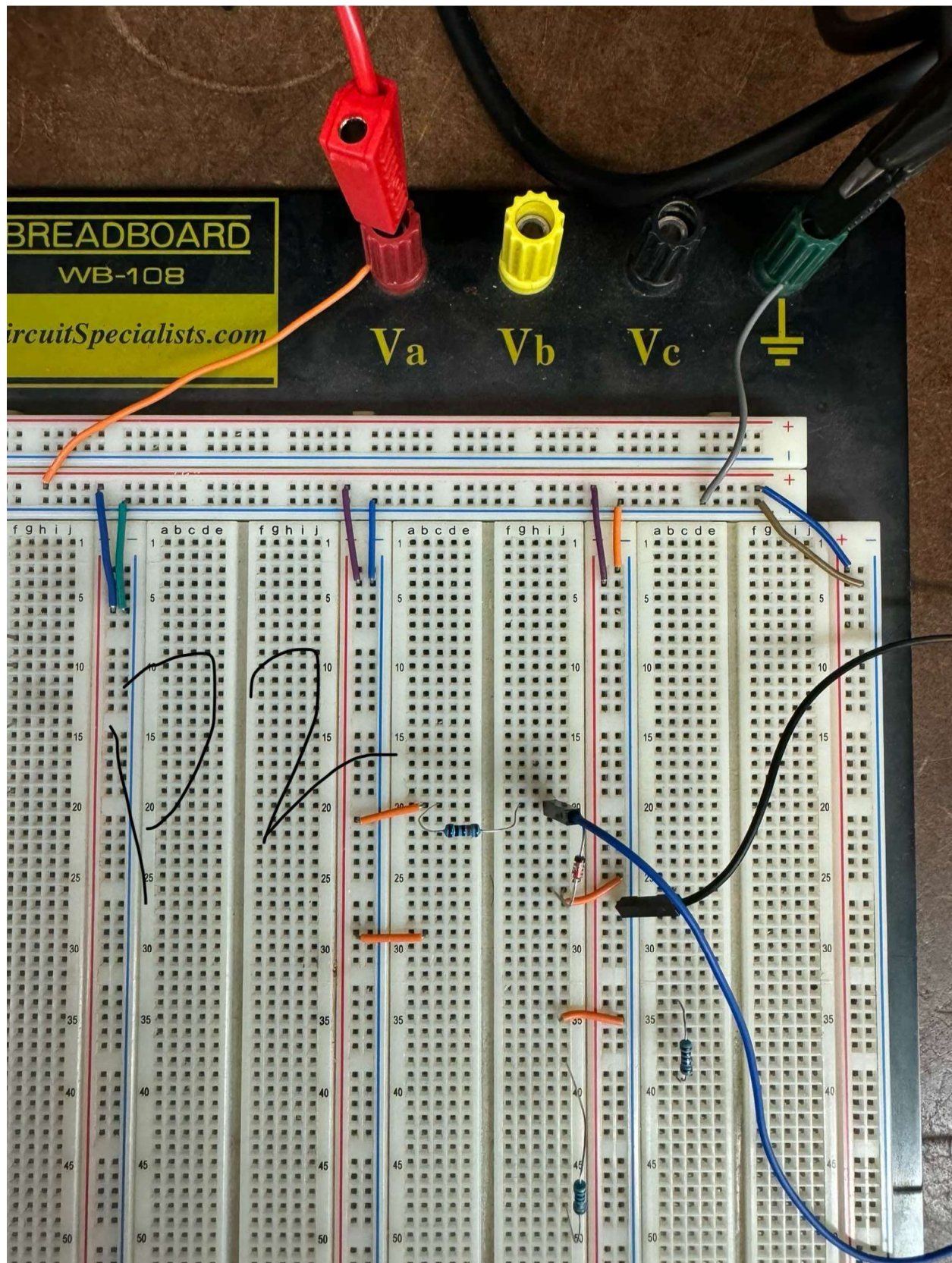

Part 4

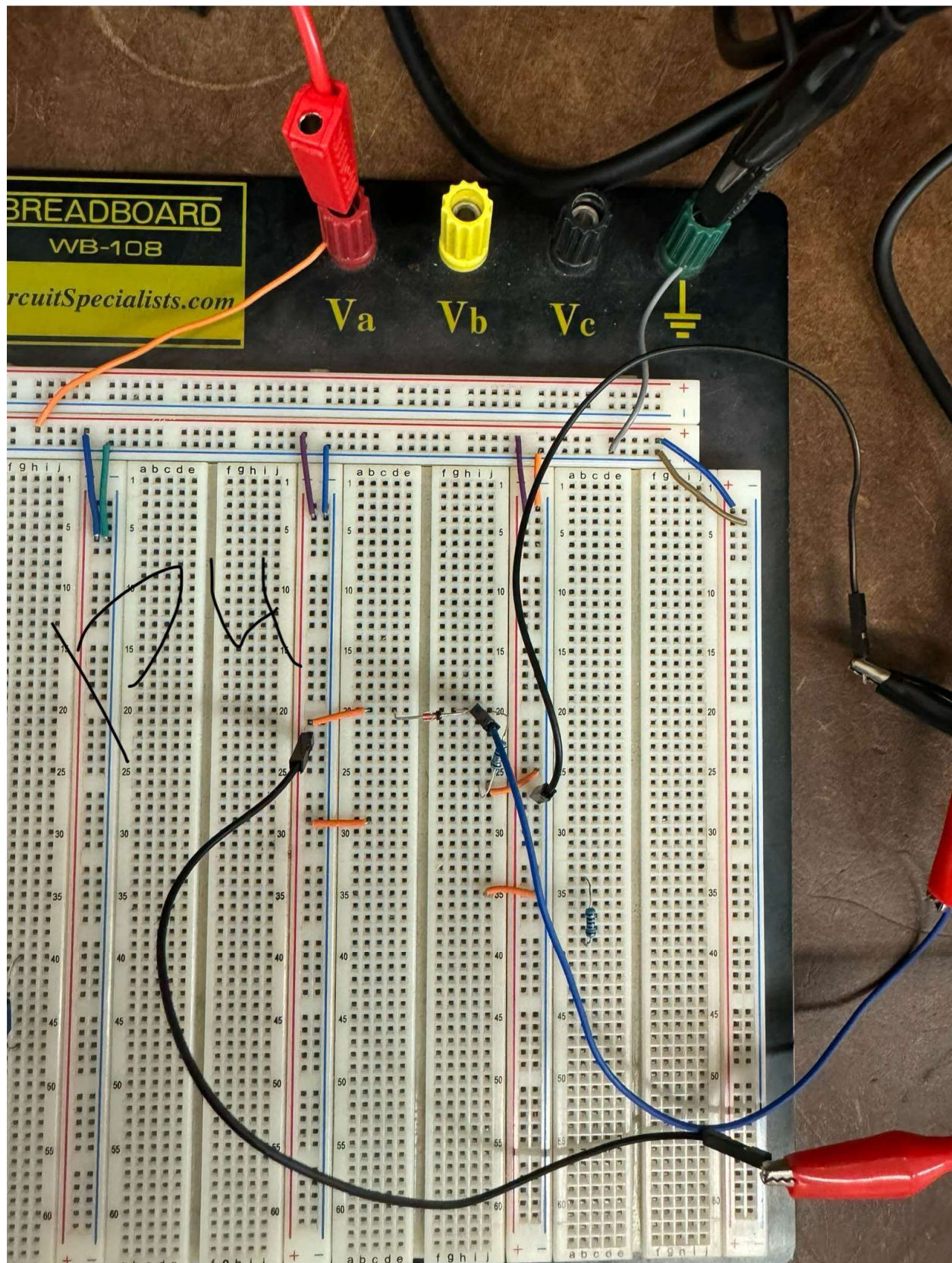

Post-Lab:

To get both the Ideality factor n and I_s , we would need to have 2 equations with 2 unknowns from our data

$$\text{Equation 1 \& 2: } I_{D1|2} = I_s e^{\frac{V_{D1|2}}{\mu V_T}}$$

$$\frac{I_{D1}}{I_{D2}} = e^{\frac{V_{D1} - V_{D2}}{\mu V_T}}$$

$$n = \frac{V_{D1} - V_{D2}}{V_T \ln\left(\frac{I_{D1}}{I_{D2}}\right)}$$

$$V_S = 1V \text{ and } 10V$$

$$n_{ze} = \frac{0.57501 - 0.66101}{26mV \times \ln\left(\frac{4.27\mu A}{0.939\mu A}\right)} = 2.18$$

$$I_s = \frac{I_D}{\frac{V_D}{e^{\mu V_T}}} = \frac{4.27\mu A}{\frac{0.57501}{e^{2.18 \times 26mV}}} = 1.67 \times 10^{-10} = 0.167nA$$

Conclusion:

In this lab, we explored the current-voltage (I-V) characteristics of Zener diodes, focusing on understanding the diode's behavior under both forward and reverse bias conditions. We utilized PSpice to perform a DC sweep, which allowed us to observe the Zener diode's response to varying current sources. The XY mode of the oscilloscope was also employed to display the I-V characteristics graphically, facilitating real-time monitoring of the diode's behavior. By analyzing our experimental data, we were able to determine key parameters such as the reverse saturation current (I_s) and the ideality factor (μ) of the Zener diode. These values were derived by comparing the forward and reverse bias characteristics, highlighting the diode's efficient

performance in regulating voltage. This experiment reinforced our understanding of Zener diodes' practical applications in circuits where voltage regulation and control are crucial.