



Electrical and Computer Engineering Department

Written by:

Group K

Brandon Contreras

Daniele Ricciardelli

ECE 2200L:

Experiment Number 13 & 14

MOSFET Self Biasing

Professor Mostafa Yazdy

Fall 2024

Thursday

December 6<sup>th</sup>, 2024

### Background Information:

The metal-oxide-semiconductor field-effect transistor (MOSFET) is a type of field-effect transistor (FET) that is typically produced through the controlled oxidation of silicon. It features an insulated gate, with its voltage controlling the device's conductivity. MOSFETs are widely employed in various amplifiers and logic gates.

### Objective:

To experiment on design, construction, and analysis of the biasing circuit for a MOS field effect transistor common source amplifier & to experiment on design and analysis of common source amplifier.

### Pre-Lab:

1. The circuit shown in Figure 1 is for a Common Source MOSFET Amplifier. By hand calculation, find  $R_D$ ,  $R_S$ ,  $R_1$ , and  $R_2$  such that the MOSFET has a Q-point of:


$$I_D = 5\text{mA}$$

$$V_{DS} = 5\text{ V}$$

Power supply voltage is  $V_{DD} = 10\text{ V}$ .

(For  $K$  and  $V_{th}$  use the values from experiment 10)

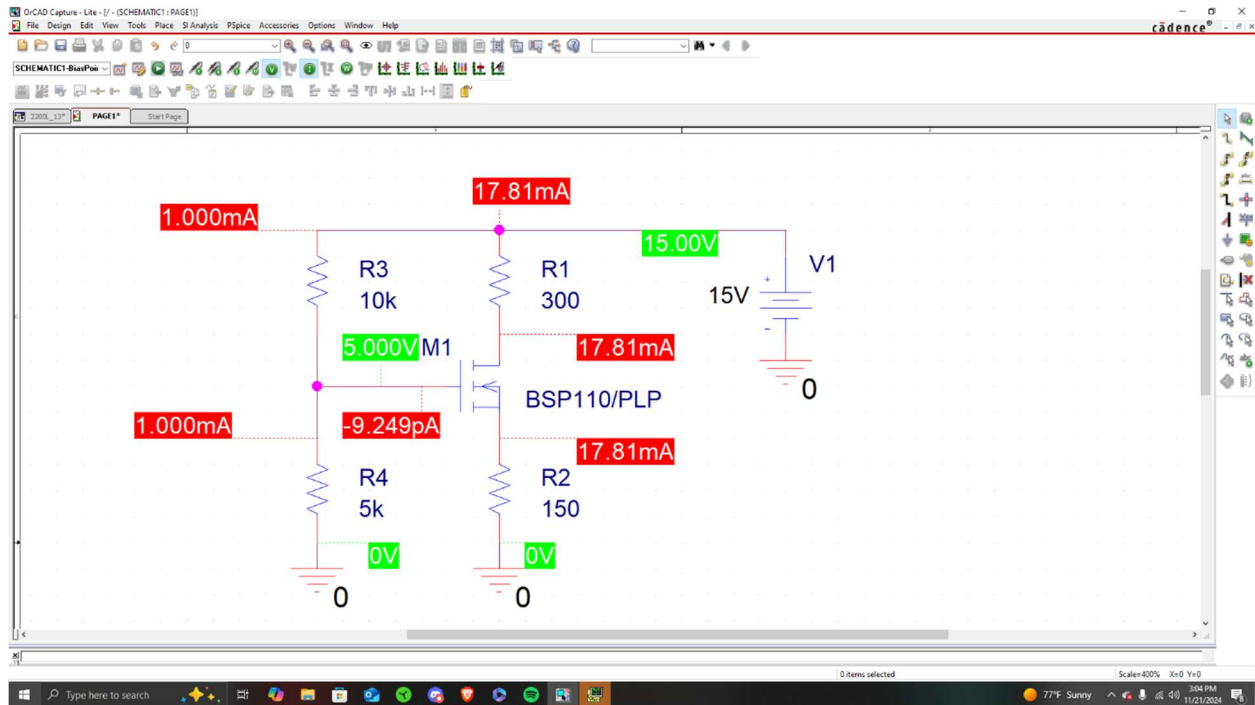2. Capture circuit A (Self-Biased Circuit, given in the lecture notes) in PSpice. Run Bias Point simulation to find all voltages and currents.



DC analysis

\*Given  $V_t = 1.7V$  n  $K_n = 0.12$

$$10^{-5} / R_d + R_5 = I_d \rightarrow R_d + R_5 = 1K \text{ Ohms} \rightarrow 500 \text{ Ohms each } (R_d \text{ n } R_5)$$

$$V_{gs} - 1.7 = \sqrt{0.005 * 2 / 0.12} - 1.99 \text{ Volts} \rightarrow V_{gs} = V_g - V_s = 1.99 - 2.5 = \sim 4.5 \text{ Volts}$$

$$-(I_{r2} * R_2) + V_{gs} + I_d R_5 = 0$$

$$10 / R_1 + R_2 = 0.0005 \rightarrow R_1 + R_2 = 20k$$


$$4.5 = 1 - * R_2 / 20k \rightarrow R_2 = 9k \rightarrow R_1 = 11k$$

Thus, R between 50k – 100k

$R_1 = 55k \text{ Ohms}$  &  $R_2 = 45k \text{ Ohms}$

### Lab Report #13:

#### 1. Figure 1:

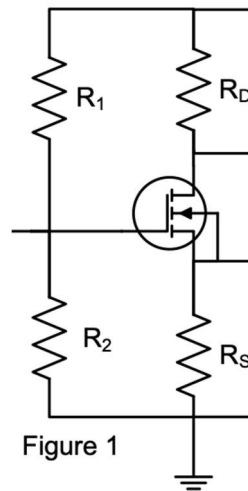

#### Part 1:

Hand Calculations:

$$V_{DD} = 10V$$

$$I_D = 5mA$$

$$V_S = 1.98V$$


$$V_{DS} = 5V$$

$$R_S = 400\Omega$$

$$R_D = 600\Omega$$

$$R_1 = 100k\Omega$$

$$R_2 = 66k\Omega$$

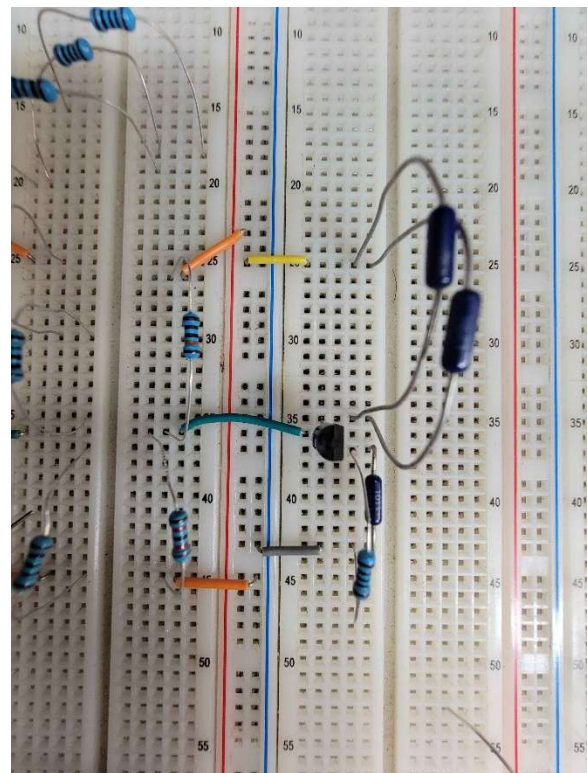

### Measured Values:

$$V_S = 2.2V$$

$$V_{DS} = 5.22V$$

$$V_{GS} = 2.11V$$

$$I_D = \frac{V_{RD}}{R_D} = 0.00478A$$

### Part 2:

Hand Calculations:

$$R_1 = 10k\Omega$$

$$R_2 = 5k\Omega$$

$$R_D = 300\Omega$$


$$R_S = 150\Omega$$

$$V_{DD} = 15V$$

$$V_{DS} = 6V$$

$$V_{GS} = 1.98V$$

$$I_D = \frac{V_{RD}}{R_D} = 0.02A$$

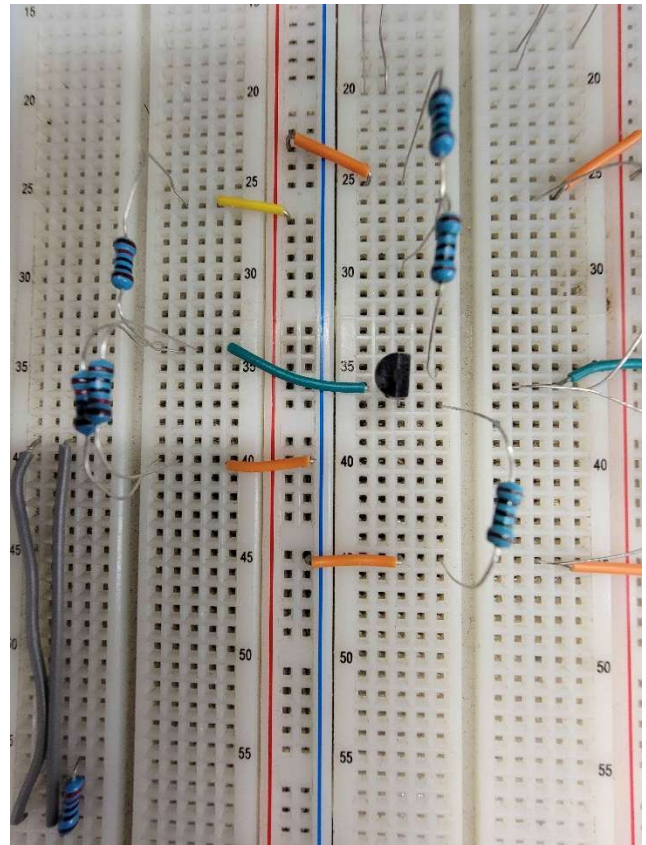

### **Calculations:**

- Calculating K Value:

$$\text{Part 2: } K = \frac{2I_D}{(V_{GS} - V_{TH})^2} = 0.69$$

Measured values (PSpice)

$$V_{DS} = 6.9855V$$

$$V_{GS} = 2.3286V$$

$$I_D = \frac{V_{RD}}{R_D} = 0.01781A$$



### **Data Analysis:**

	Vgs	Vds	Id			Vgs	Vds	Id
Measured	2.11	5.22	0.00478		Measured	1.98	6	0.02
Hand Calc	1.98	5	0.005		PSpice	2.3285	6.9855	0.01781
Deviation	6.356968	4.305284	4.498978		Deviation	16.17732	15.17847	11.58424

Where deviation is in %

## Lab Report #14:



### Part 1:

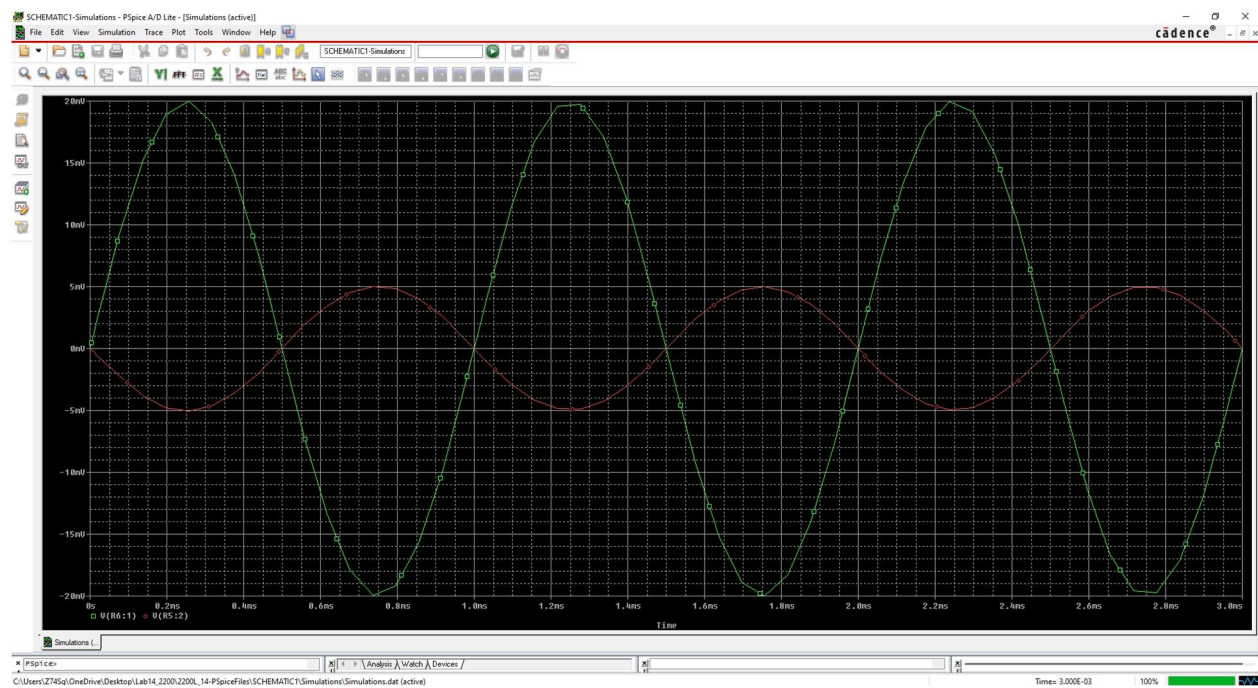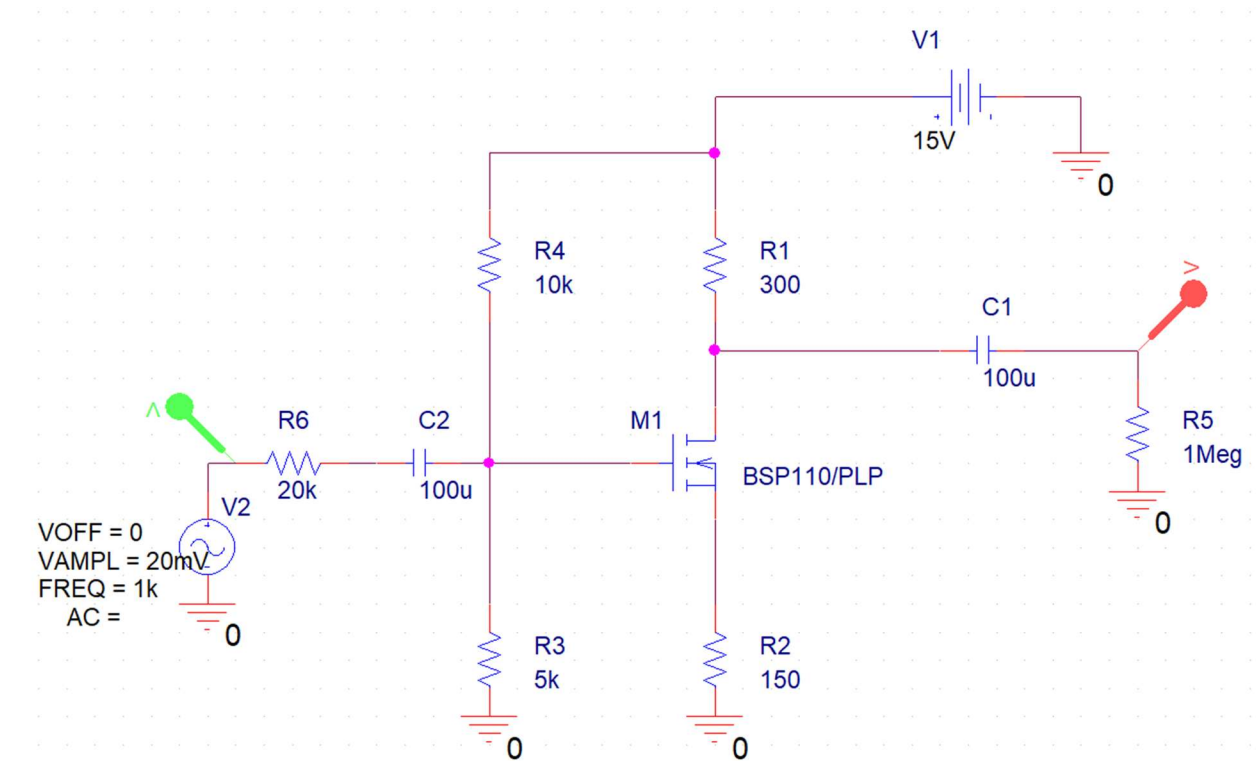

$$\text{Gain} = 0.5$$





## Part 2:

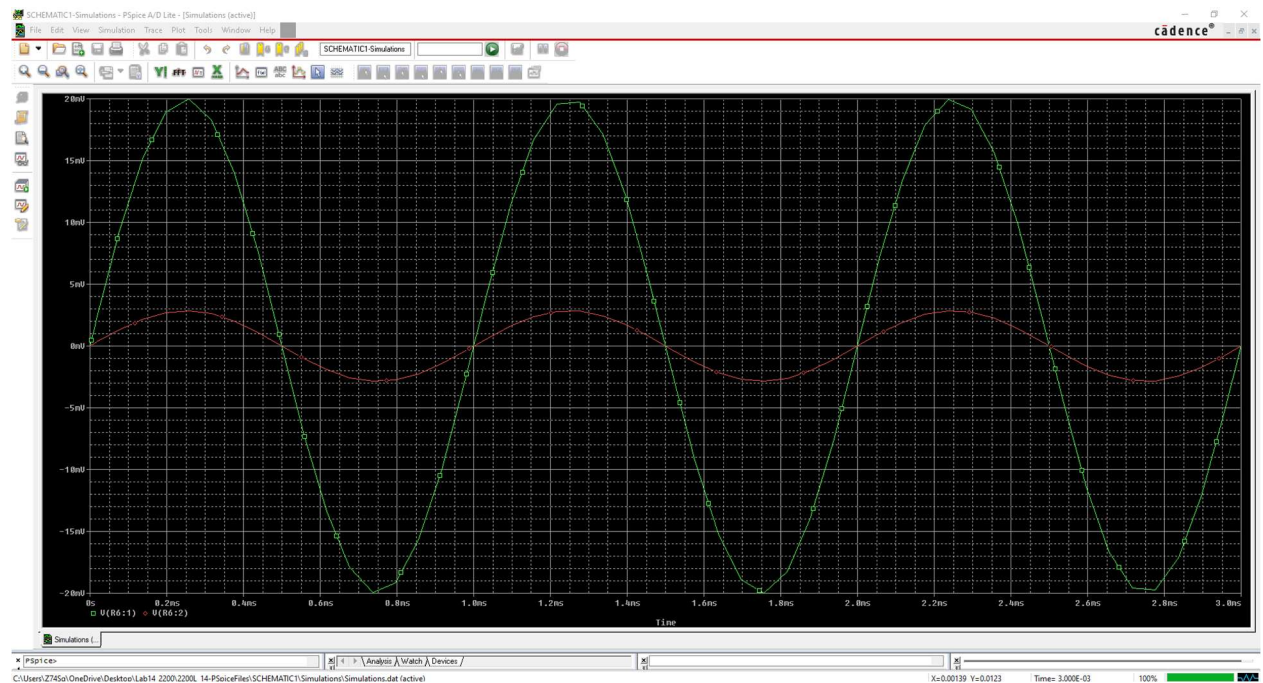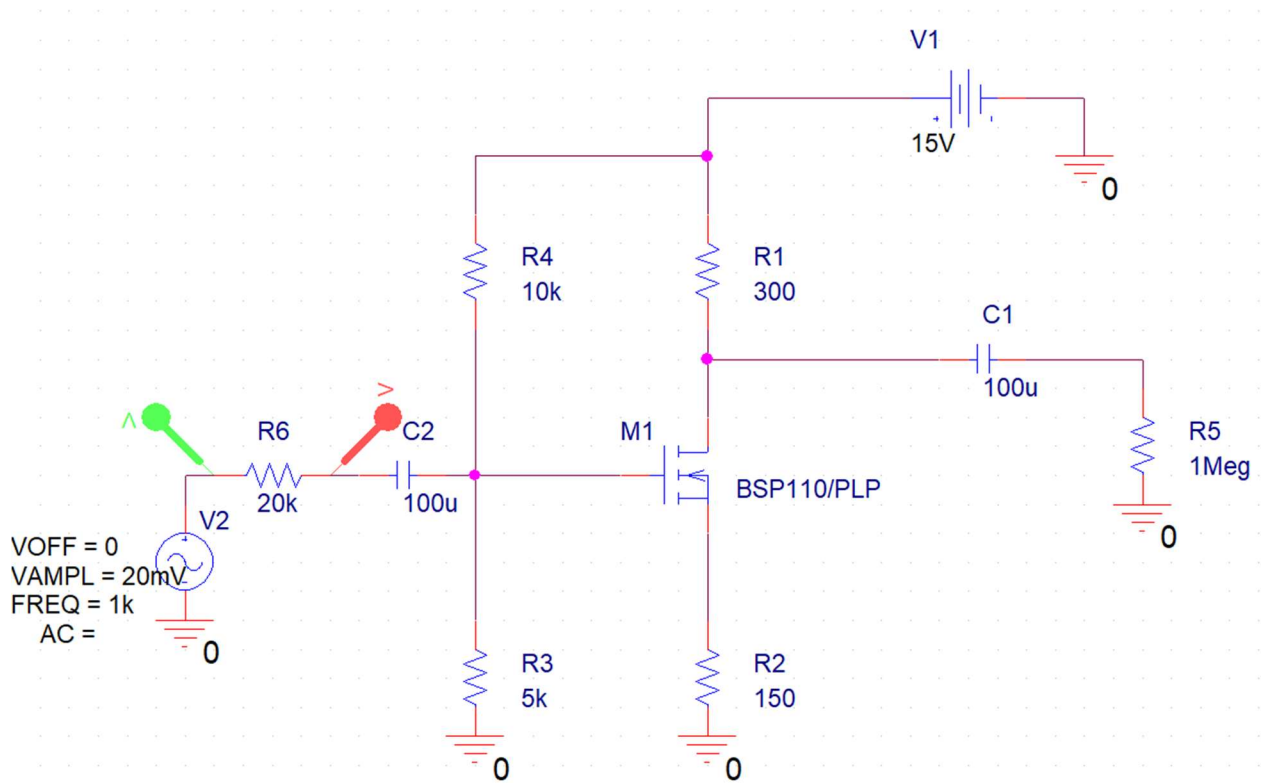



### Part 3:

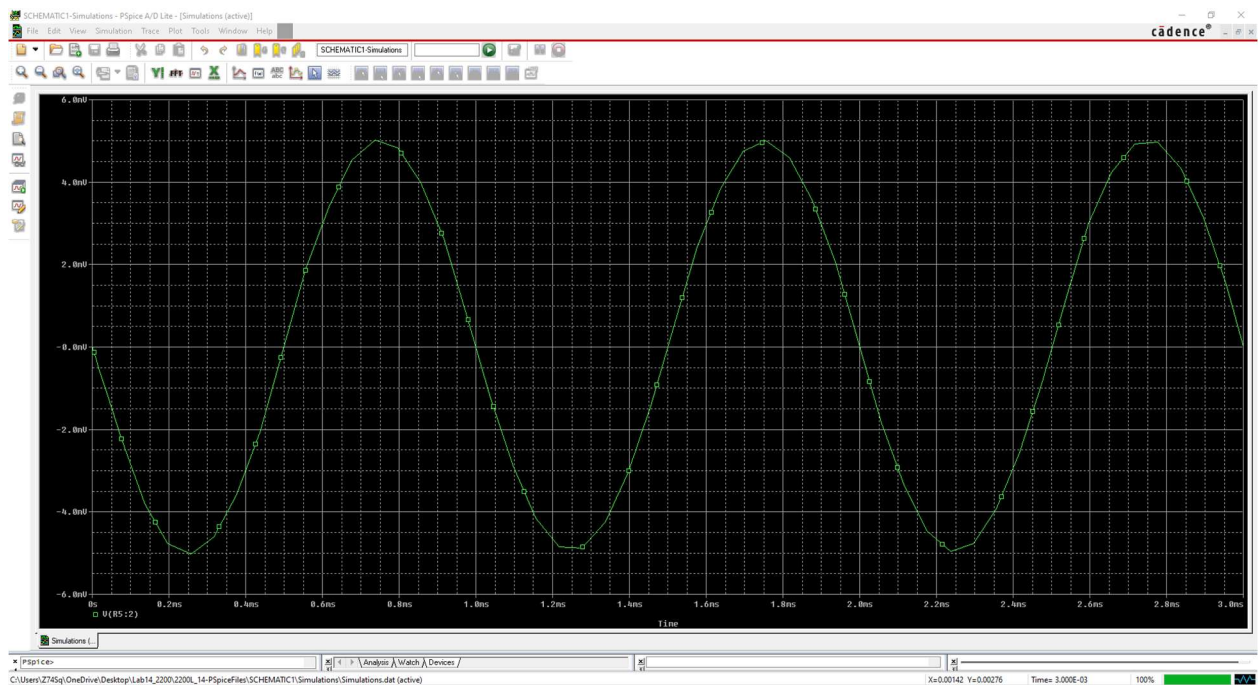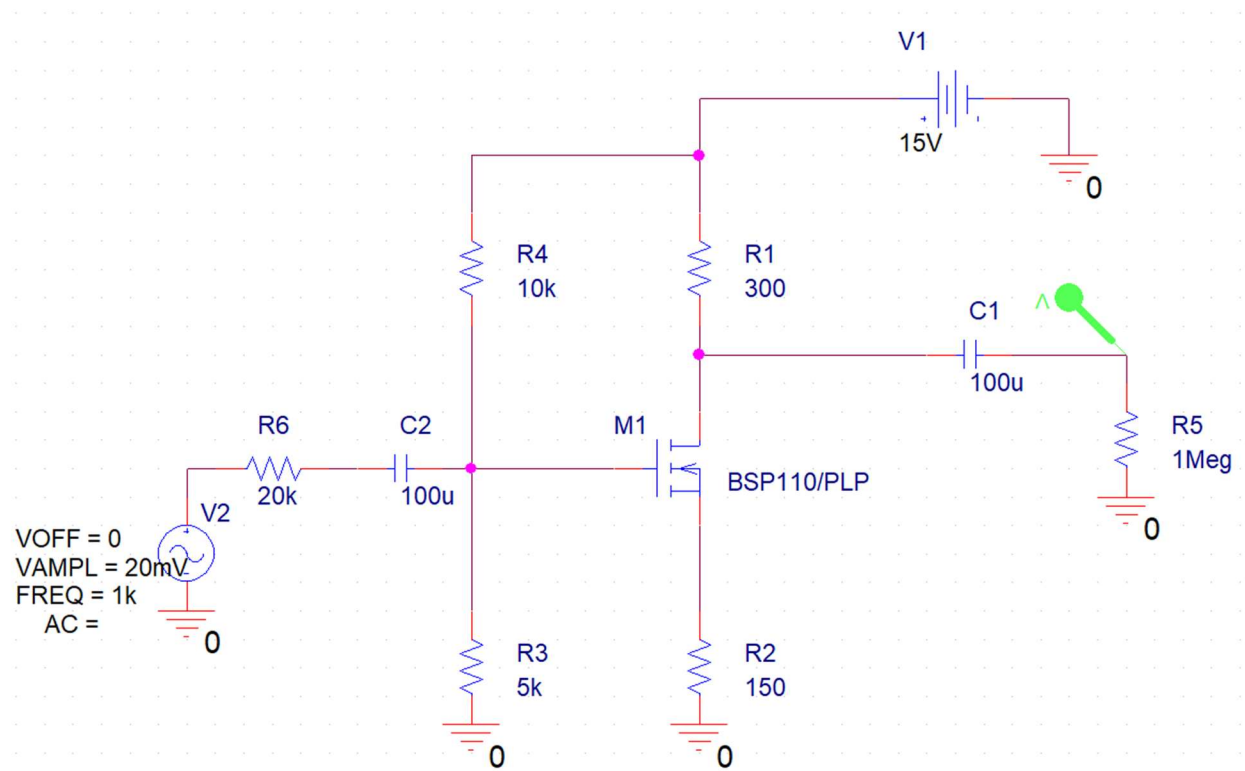

**Calculations:**

$$V_s = 20\text{mV} \quad V_i = 19.711 \text{ mV} \quad R_{in} = 20\text{kOhms}$$

$$R_i = V_i * R_{in} / V_s - V_i \quad \text{where } V_s - V_i = 0.000289 \quad \rightarrow \quad R_i = 394.22 / 0.00289 = 1.36\text{M Ohms}$$

$$V_o' = V_o * R_L / R_L + R_o \quad \rightarrow \quad R_o = 600 * ( 466.779 - 233.664 / 233.664 )$$

$$\rightarrow \quad R_o = 600 * 0.9977 = 598.22 \text{ Ohms}$$

$$A_v = V_{pp}(V_o) / V_{pp}(V_i) = 884.779 / 39.847 = 22.2$$

### Conclusion:

In this experiment, we successfully explored the design, construction, and analysis of a MOSFET self-biasing circuit and its application in a common source amplifier. By performing both hand calculations and simulations in PSpice, we gained a deeper understanding of how the biasing point is influenced by resistor values, input voltage, and circuit parameters. These insights are crucial for designing stable amplifiers with desired characteristics. The experimental results, compared to theoretical values, highlighted the practical considerations and potential deviations inherent in real-world implementations. This foundational knowledge will be instrumental in designing and optimizing amplifiers in future applications.